

15/06/26 Day 20 kamineni Dhana Sri keerthi

option 02


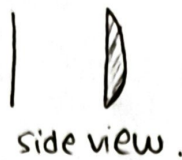
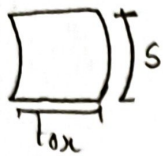


Diagram $\rightarrow$ refer Day 18.

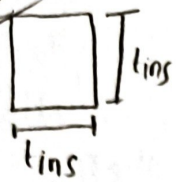Assuming the current is distributed uniformly over cross section of pin hole. [bent rectangular prism]



$L_p \rightarrow$ Total height of pinhole [BRP]

$tox \rightarrow$ thickness (radical width)

$S \rightarrow$ Arc length

$J \rightarrow$ Current density.

Inductance of finite thin sheet.

3 Cross sectional Area outer bent rectangular prism

$$A = S L_p \text{ (m}^2\text{)}$$

$$S = \theta [tox + r_{TSV}] \text{ (m)}$$



$$S = \frac{\pi}{2} (0.13 + 2.47) \text{ um.}$$

4 The total self inductance of a uniform conductor

$$L_{\text{sh}} = L_{\text{int}} + L_{\text{ext}}$$

5 At high frequency



calculating inductance of finite thin sheet.

$\rightarrow$ Why we are taking inductance of thin sheet instead of entire 3D mode

$$tox = 0.13 \text{ um. } S = 4.08 \text{ um. } L_p = 4 \text{ um.}$$

Ans: In semiconductor tech, tox is usually $\ll$ often, but. L_p and S are typically much larger.

Because tox is so small compared to other two dimensions, the 3D volume behaves electrically almost identical to a 2D sheet.

General Lext (sheet/block finite)

$$L_{ext} = \frac{\mu_0 t}{2\pi} \left[\ln \left[\frac{2(l+w)}{t} \right] + \frac{1}{2} \right] \quad (H) \rightarrow \text{Grover's Inductance calculations.}$$

General Lint

$$L_{int} = \frac{\mu_0 t}{3(l+w)}$$

(So when current direction (F) is much smaller than cross section dimensions (l and w) the Neumann integral for external flux simplifies to.)

Now our model

→ good books.

$$L_{ext} = \frac{\mu_{TSV} t_{ox}}{2\pi} \left[\ln \left[\frac{2(l_p+s)}{t_{ox}} \right] + \frac{1}{2} \right]$$

$$L_{int} = \frac{\mu_{TSV} t_{ox}}{3(l_p+s)}$$

$$L_{ext} = \frac{\mu_0 \text{path}}{2\pi} \left[\ln \left[\frac{2 \pi \mu_{TSV} t_{ox}}{\text{path}} \right] + \frac{1}{2} \right]$$

$$L_{ext} = \frac{\mu_0 \text{path}}{3(\text{perimeter})}$$

$$\frac{\mu_{TSV}}{\sqrt{l_p^2 + t_{ox}^2}}$$

$$\frac{0.5 \mu}{\sqrt{(u^2 \mu + (0.5)^2) \mu}}$$

$$L = L_{ext} + L_{int}$$

Proposed model.

$$L_{SH} = \frac{\mu_{TSV} t_{ox}}{2\pi} \left[\ln \left[\frac{2(l_p+s)}{t_{ox}} \right] + \frac{1}{2} \right] + \frac{\mu_{TSV} t_{ox}}{3(l_p+s)}$$

Novel model

$$L_{SH} = \mu_{TSV} t_{ox} \left[\cosh^{-1} \left[\frac{S}{\sqrt{l_p^2 + s}} - \sqrt{t_{ox}^2 + l_p^2 + s^2} + \frac{S}{4} + \sqrt{l_p^2 + s^2} \right] \right]$$

15/06/26 Day 20 kamineni Dhana Sri Keerthi

Defected Trv (R_{sht}, L_{sht})

RLGC $\rightarrow$ same as defect free.

Novel model:- (final)

$$R_{sht} = \frac{P_T \cdot t_{ox}}{L_s^2}$$

$$L_{sht} = \frac{\mu_0 \mu_{Trv} t_{ox}}{2\pi} \left[\cosh^{-1} \left(\frac{t_{in} s}{\sqrt{L_s^2 + t_{in} s^2}} - \sqrt{2 t_{in} s^2 + L_s^2} + \frac{t_{in} s}{4} + \sqrt{L_s^2 + t_{in} s^2} \right) \right]$$

Proposed model

$$R_{sht} = \frac{P_T t_{ox}}{L_p (r_{Trv} + t_{ox}) \theta}$$

$$L_{sht} = \frac{\mu_0 \mu_{Trv} t_{ox}}{2\pi} \left[\cosh^{-1} \left(\frac{s}{\sqrt{L_p^2 + s^2}} - \sqrt{t_{ox}^2 + L_p^2 + s^2} + \frac{s}{4} + \sqrt{L_p^2 + s^2} \right) \right]$$

126, Day 20 kamineni Dhana Srikeerthi


TSV models

Defect free

Defected CG [Chao liu Proposed]

Defected RL [Novel paper proposed]

Defected Circuit.

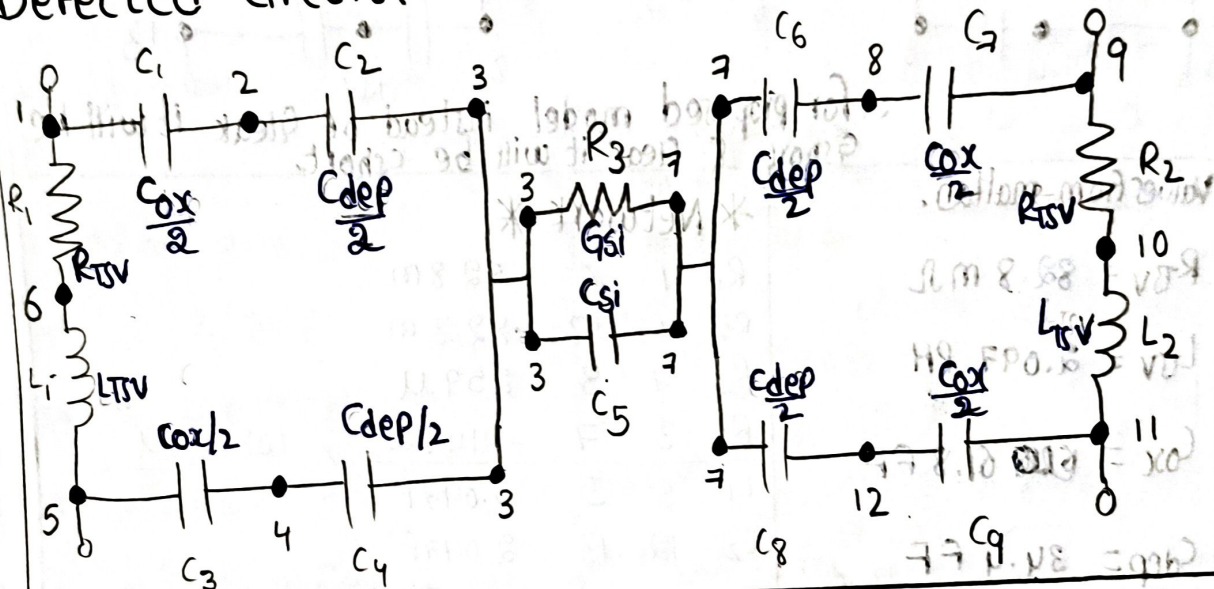

Values from matlab.

$$R_{TSV} = 82.8 \text{ m}\Omega$$

$$L_{TSV} = 2.097 \text{ PH}$$

$$C_{ox} = 65.07 \text{ FF}$$

$$C_{dep} = 35.84 \text{ FF}$$


$$G_{si} = 354 \text{ }\mu\text{S}$$

$$C_{si} = 3.73 \text{ FF}$$

* Network *

R_1	1	6	82.8 m
R_2	9	10	82.8 m
R_3	3	7	2354 μ
L_1	6	5	2.097 P
L_2	10	11	2.097 P
C_1	1	2	32.53 F
C_2	2	3	17.92 F
C_3	5	4	32.53 F
C_4	4	3	17.92 F
C_5	3	7	3.73 F
C_6	7	8	17.92 F
C_7	8	9	32.53 F
C_8	7	12	17.92 F
C_9	12	11	32.53 F.

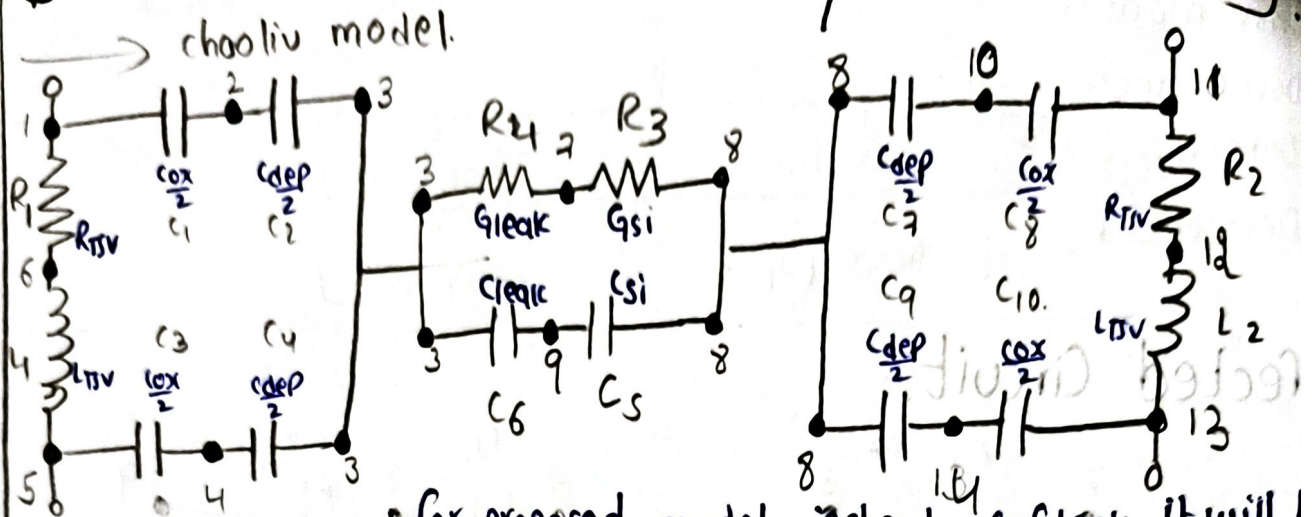Defected CG. [chao liu model / Proposed model]



Values from matlab.

$$R_{TV} = 82.8 \text{ m}\Omega$$

$$L_{TV} = 2.097 \text{ PH}$$

$$C_{ox} = 61.8 \text{ FF}$$

$$C_{dep} = 34.4 \text{ FF}$$

$$C_{si} = 2.73 \text{ FF}$$

$$G_{leak} = 64.0 \text{ FF}$$

$$G_{si} = 259 \mu S$$

$$G_{leak} = -214.3 \mu S$$

$$G_{short} = 108.4 \mu S$$

$$C_{short} = 14.09 \text{ FF}$$

* Network *

R_1	1	6	82.8 m
R_2	11	12	82.8 m
R_3	7	8	259 μ
R_4	3	7	-214.3 μ / 108.4 μ

$$L_1 \quad 6 \quad 5 \quad 2.097 \text{ P}$$

$$L_2 \quad 12 \quad 13 \quad 2.097 \text{ P}$$

$$C_1 \quad 1 \quad 2 \quad 30.9 \text{ F}$$

$$C_2 \quad 2 \quad 3 \quad 17.2 \text{ F}$$

$$C_3 \quad 5 \quad 4 \quad 30.9 \text{ F}$$

$$C_4 \quad 4 \quad 3 \quad 17.2 \text{ F}$$

$$C_5 \quad 9 \quad 8 \quad 2.73 \text{ F}$$

$$C_6 \quad 3 \quad 9 \quad 64.0 \text{ F}$$

$$C_7 \quad 8 \quad 10 \quad 17.2 \text{ F}$$


$$C_8 \quad 10 \quad 11 \quad 30.9 \text{ F}$$

$$C_9 \quad 8 \quad 14 \quad 17.2 \text{ F}$$

$$C_{10} \quad 14 \quad 13 \quad 30.9 \text{ F}$$

$$0.007 \times 10^{22} \text{ H}$$

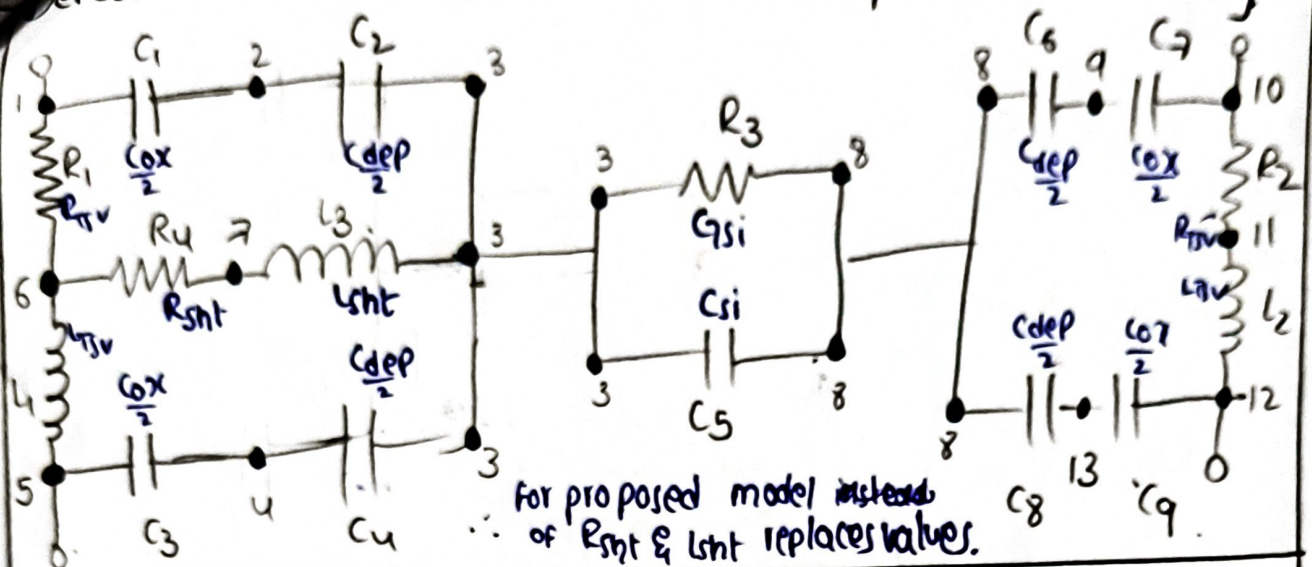Defected RL [Novel proven model / proposed model]



Values from matlab.

$$R_{SV} = 82.8 \text{ m}\Omega$$

$$L_{SV} = 2.097 \text{ pH}$$

$$C_{ox} = 65.07 \text{ fF} \quad 32.53 \text{ f}$$

$$C_{dep} = 35.84 \text{ fF} \quad 17.92 \text{ f}$$

$$C_{si} = 3.73 \text{ fF}$$

$$G_{si} = 354 \text{ }\mu\Omega$$

→ Novel model

$$R_{sh} = 0.136 \text{ m}\Omega$$

$$L_{sh} = 11.9011 \times 10^{-21} \text{ H}$$

→ Proposed model

$$R_{sh_p} = 0.133 \text{ m}\Omega$$

$$L_{sh_p} = 20.508 \times 10^{-21} \text{ H}$$

* Network *

R_1	1	6	82.8 m
R_2	10	11	82.8 m
R_3	3	8	354 $\mu\Omega$
R_4	6	7	0.136 m / 0.133 m
L_1	6	5	2.097 p
L_2	11	12	2.097 p
L_3	7	3	11.901e-20 / 2.05e-20
C_1	1	2	32.53 f
C_2	2	3	17.92 f
C_3	5	4	32.53 f
C_4	4	3	17.92 f
C_5	3	8	3.73 f
C_6	8	9	17.92 f
C_7	9	10	32.53 f
C_8	8	13	17.92 f
C_9	13	12	32.53 f

ent have ~~sharp~~ spikes. what does this mean.

effect free TSV

- 3.a $\rightarrow$ negligible delay, almost no distortion.
- 3.b $\rightarrow$ 1 exhibit short +ve & -ve spikes during switching
because The TSV capacitance charges & discharges.
- 2 The +ve spikes correspond to charging events
-ve " " " dis " "
- 3 The similarity btw J_p and Q_p ~~I~~ states that
TSV introduces minimal additional losses.

How these currents can reduce.

1 $\downarrow$ parasitic Capacitance and inductance.



$\downarrow$ use $\downarrow$ low dielectr.

TSV diameter

$J =$ leakage factor $\frac{\text{damage area}}{\text{side wall area}}$

why rise and ~~all~~ negative

Rise time $\uparrow$

because

charging C

takes long time

Fall time $\downarrow$

discharging
fast.

